

**HACETTEPE UNIVERSITY**  
**DEPARTMENT OF COMPUTER ENGINEERING**  
**BBM436 MICROPROCESSORS LAB.**

Assoc. Prof. Dr. Harun ARTUNER,  
Ali Osman SERHATOGLU, Burcu YALÇINER  
17.11.2020


**ASSIGNMENT 4**

**Topic**

*Submit your work file by attaching it to your report.*

**Phase 1**

Perform the address map given below for the memory units you used in previous studies. Implement the necessary address decoding circuits on the proteus for this.

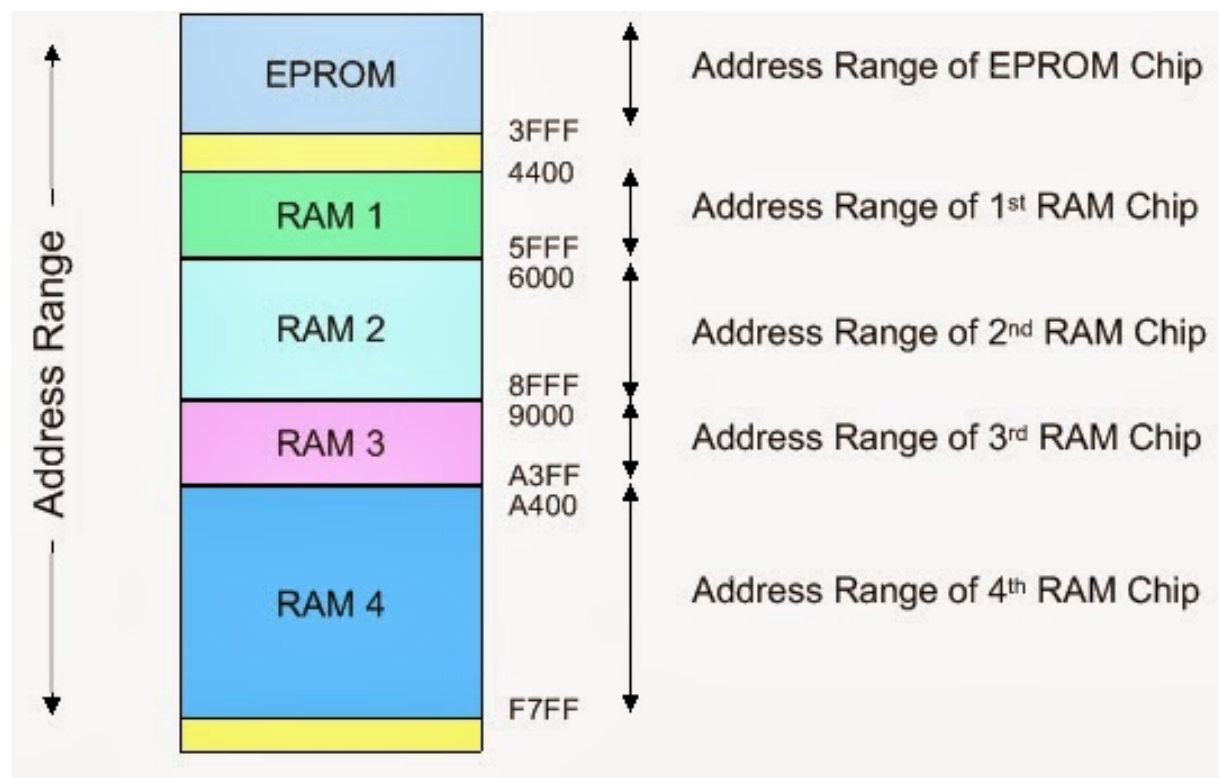

**Phase 2**

Create the necessary prerequisites for the system to work. Provide these in detail in your report.

**Phase 3**

Again, Draw the time plot of the address, data and control paths on the virtual logic analyzer in a setup.